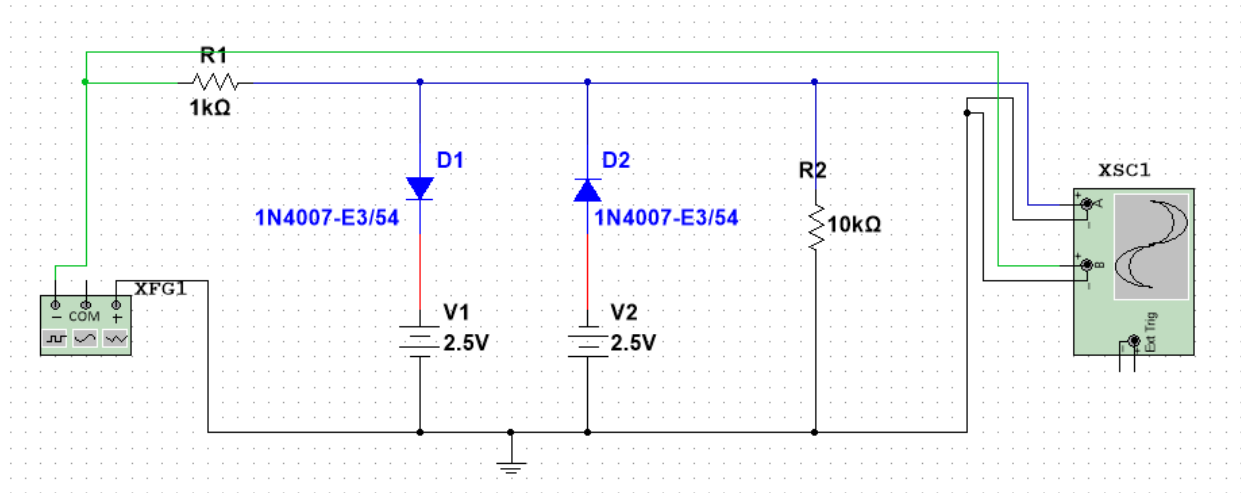


DOUBLE ENDED CLIPPERS

CIRCUIT DIAGRAM



Platform Used

The circuit is designed and simulated using **Multisim**, a widely used electronic circuit simulation software. It allows virtual testing of analog circuits using realistic components such as signal generators, diodes, resistors, DC sources, and oscilloscopes.

Components Used

1. AC Signal Generator (XFG1)

- Generates the input sinusoidal waveform.
- Provides an alternating voltage that is applied to the clipper circuit.
- The amplitude and frequency can be adjusted as required.

2. Resistor R1 (1 kΩ)

- Connected in series with the input signal.
- Limits the current flowing through the diodes.
- Protects the diodes from excessive current.

3. Diodes D1 and D2 (1N4007)

- Silicon PN junction diodes.
- Used for clipping the positive and negative portions of the input signal.

4. DC Bias Sources V1 and V2 (2.5 V each)

- Provide biasing to the diodes.
- Set the clipping levels for both positive and negative halves of the waveform.

- Make the clipper a **biased double-ended clipper**.

5. Resistor R2 (10 kΩ)

- Acts as the load resistor.
- Output voltage is measured across this resistor.

6. Oscilloscope (XSC1)

- Displays the input and output waveforms.
- Used to observe the clipping action clearly.

Basic Working of the Double Ended Clipper Circuit

A **double ended clipper circuit** limits both the **positive and negative peaks** of an input signal beyond predefined voltage levels.

Positive Half Cycle

- When the input voltage exceeds + (2.5 V + diode drop):
 - Diode **D1 becomes forward biased**.
 - Excess voltage is diverted through D1 and V1 to ground.
 - The output voltage is clipped at the positive level.

Negative Half Cycle

- When the input voltage goes below – (2.5 V + diode drop):
 - Diode **D2 becomes forward biased**.
 - Excess negative voltage is diverted through D2 and V2.
 - The output voltage is clipped at the negative level.

Output Observation

- The output waveform appears **flattened at both top and bottom**.
- This confirms that both positive and negative peaks are clipped.
- The clipping levels are determined by the **bias voltages and diode drops**.

Conclusion

This circuit demonstrates the working of a **biased double ended clipper** using diodes. By applying suitable DC bias voltages, the amplitude of an AC signal can be limited on both sides. Such circuits are commonly used in **signal conditioning, over-voltage protection, and waveform shaping applications**.